

Quiz (7)

Prepared by: Dr. Hessa Al-Junaid


4th December 2012

Time duration: 8 minutes

Implement the following function using 3-to-8 line decoder and AND gate:

$$f(A, B, C) = \sum m(0, 1, 4, 7)$$

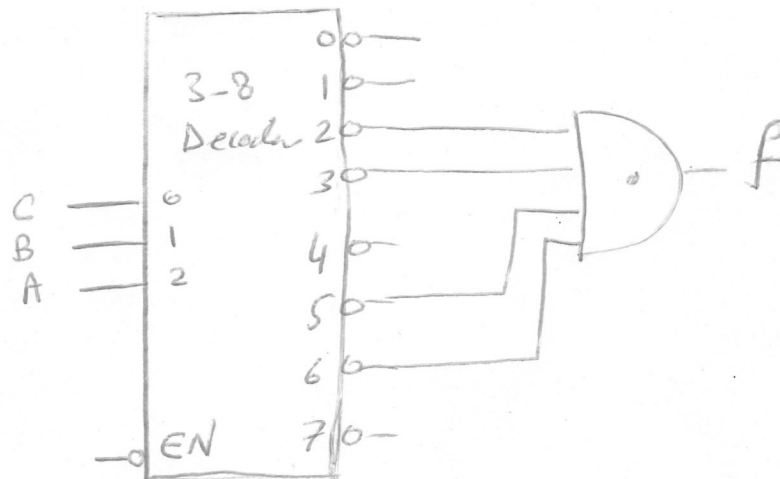Active Low Decoder + AND \rightarrow Maximum Expansion
 $f(A, B, C) = \prod M(2, 3, 5, 6)$ (5)



active low (2)

circuits (3)